



LINCOLN
UNIVERSITY
COLLEGE

Sheet 0 of 5

Code: DEE 4544

ASSIGNMENT (15%)

Faculty : ENGINEERING

Course : DIPLOMA ELECTRICAL AND ELECTRONICS ENGINEERING (ODL)

Module Title : DIGITAL ELECTRONICS

Date : 2nd MAY 2024

Instruction to candidates

1. Answer ALL the questions.

CO	Descriptions	Domain
CLO 2	Use DeMorgans Theorem to simplify a negated expression. (C3, PLO2)	C3
CLO 3	Formulate and employ a Karnaugh Map to reduce Boolean expressions and logic circuits to their simplest forms. (C2, PLO6)	C2

Do not open this question paper until instructed.

QUESTION 1

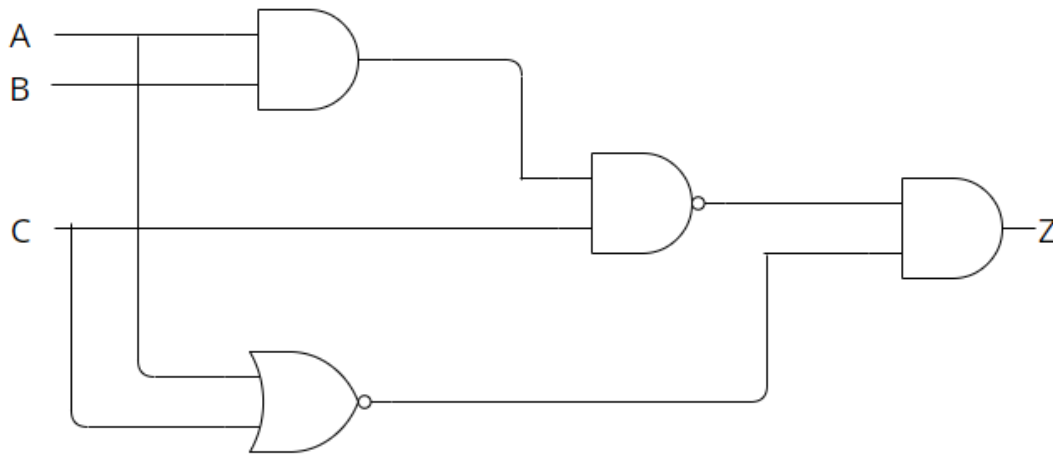


Figure 1

- List the types of gates used in the circuit shown in Figure 1. (3 Marks)
- Determine the number of input and output variables in the circuit (Figure 1). (4 Marks)
- Write the Boolean expression for Z in terms of A, B and C. (3 Marks)
- Convert the Boolean expression in (c) into Sum-of-products (SOP) form. (4 Marks)
- Construct the Truth Table for this circuit. (6 Marks)
- Simplify the Boolean expression in (c) using the K – Map technique. (6 Marks)
- Sketch the simplified circuit based on question (f). (4 Marks)

(Total = 30 Marks)

QUESTION 2

a. Answer the question based on Figure 2.

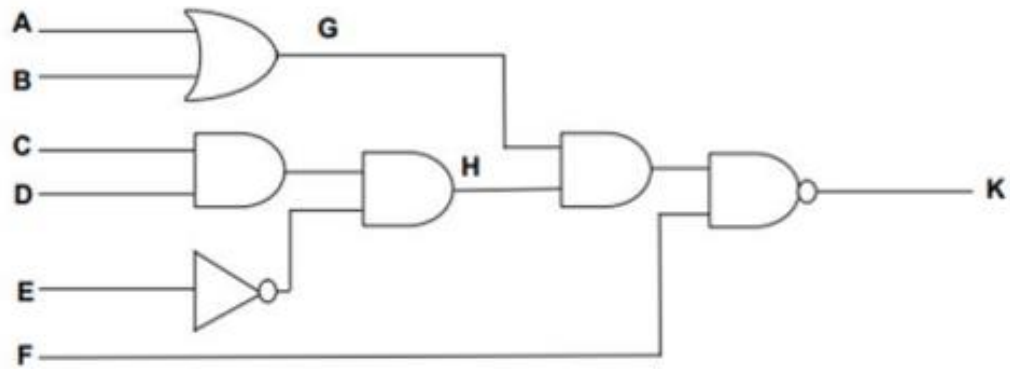


Figure 2

Complete the truth table for the inputs that have been given.

(6 Marks)

Inputs								
A	B	C	D	E	F	G	H	K
0	0	1	1	0	0			
0	1	1	1	0	1			
1	0	1	1	1	0			
1	1	1	1	1	1			

b. Figure 3 below shows a logic circuit.

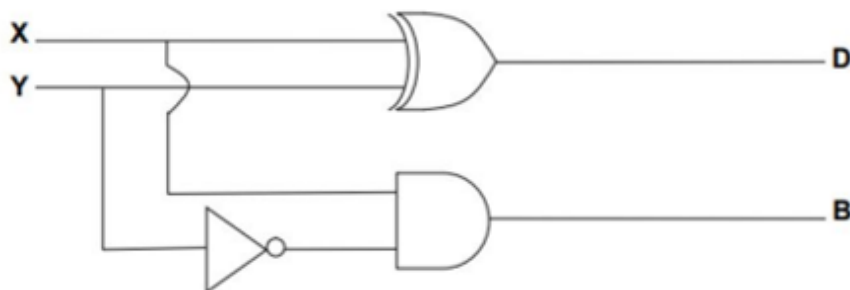


Figure 3


Based on Figure 3, write a Boolean expression for D and B.

(4 Marks)

(Total = 10 Marks)

QUESTION 3

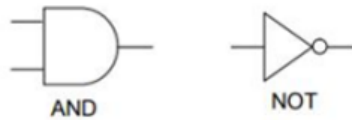- a. Represent the Boolean expression $Q = \overline{\overline{A}} \cdot \overline{\overline{B}}$ as a logic circuit by drawing a diagram in the space below using only the following symbols: (4 Marks)



- b. Use the following truth tables to demonstrate that $A + B = \overline{\overline{A} \cdot \overline{B}}$ (10 Marks)

A	B	A + B
0	0	
0	1	
1	0	
1	1	

A	B	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$\overline{\overline{A} \cdot \overline{B}}$
0	0				
0	1				
1	0				
1	1				

- c. Simplify the following Boolean expressions:

i. $x = AB + A(B + C) + B(B + C)$

(3 Marks)

ii. $x = \overline{(A + B) \cdot (\overline{C} + D)}$

(3 Marks)

(Total = 20 Marks)

QUESTION 4

- a. Complete the Boolean function that corresponds to the following truth table.

INPUT			OUTPUT
A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$X = \bar{A}.B.C +$ _____ (4 Marks)

The part to the right of the equal sign is known as the sum-of-product.

- b. For the truth table above complete the Karnaugh Map (K-map) (4 Marks)

		AB			
		00	01	11	10
C	0				
	1				


- c. Simplify the Boolean expression by group(s) of 1's to produce an optimal SOP and write the simplified SOP Boolean expression. (6 Marks)

(Total = 14 Marks)

---- END OF PAPER ----

Question 1

Digital Electronics

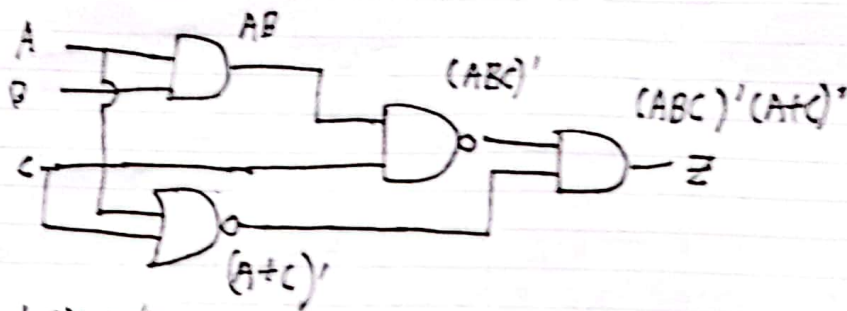

a) List logic gate

AND gate, NAND gate and NOR gate

b) Determine the input & output variable.

Input variable: A, B and C

Output variable: Z

c) Write the boolean expression for Z in terms of A, B and C

$$Z = (ABC)'(A+C)'$$

* d) Convert boolean expression in (c) to SOP form

$$\begin{aligned} Z &= (ABC)'(A+C)' \\ &= (A'+B'+C')(A'C)' \quad \rightarrow \text{De Morgan Law} \\ &= A'A'C' + A'B'C' + A'C'C' \\ &= A'C' + A'B'C' + A'C' \\ &= A'C' + A'B'C' \\ &= A'C'(1+B') \\ &= A'C' \end{aligned}$$

* e) ~~K-map technique~~ Construct the truth table for the circuit

	A	B	C	AB	ABC	(ABC)'	A+C	(A+C)'	Z = (ABC)'(A+C)'
①	0	0	0	0	0	1	0	1	1 A'B'C'
②	0	0	1	0	0	1	1	0	0
③	0	1	0	0	0	1	0	1	1 A'B'C'
④	1	0	0	0	0	1	1	0	0
⑤	1	0	1	0	0	1	1	0	0
⑥	1	1	0	1	0	1	1	0	0
⑦	1	1	1	1	1	0	1	0	0
⑧	0	1	1	0	0	1	1	0	0

f)

$\begin{matrix} A \backslash B \\ C \end{matrix}$	00	01	11	10
0	1	1	0	0
1	0	0	0	0


$$\bar{Z} = A'C'$$

$$\begin{aligned} Z &= A'B'C' + A'BC' \\ &= A'C'(B' + B) \\ &= A'C' \end{aligned}$$

proved they're same.


g) Sketch the simplified circuit based on question (f)

- NOR gate

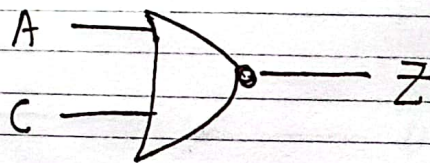


Truth table		
A	C	NOR \bar{Z}
0	0	1
0	1	0
1	0	0
1	1	0

Question 2
a)

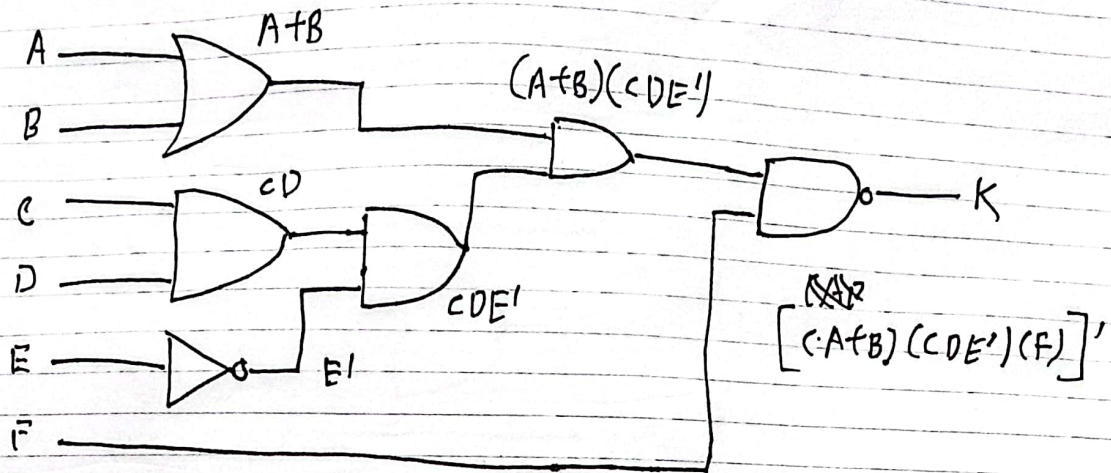

Inputs						Outputs		
A	B	C	D	E	F	$A+B$	$(C+D)E$	K
0	0	1	1	0	0	0	0	0
0	1	1	1	0	1	1	0	1
1	0	1	1	1	0	1	1	1
1	1	1	1	1	1	1	1	1

b)

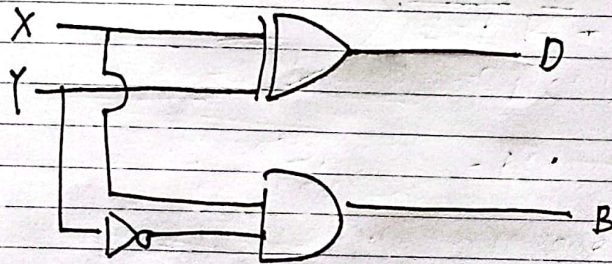

$$D = X + Y$$

$$B = XY$$

Question 3
a)

$$Q = (A'B')'$$


$$= A'' + B''$$

$$= A + B$$

OR gate

A	B	\bar{A}	\bar{B}	$\bar{A}\bar{B}$	$\overline{\bar{A}\bar{B}}$
0	0	1	1	1	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1

answer :

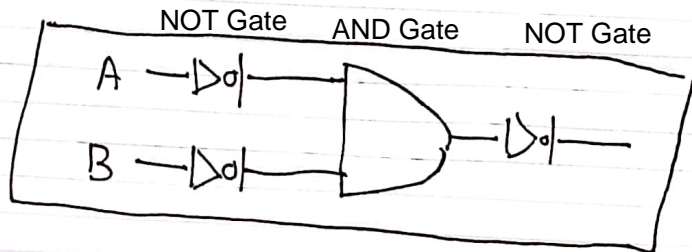

Test

Scenario 1

	NOT	AND	NOT
Input A 0	1	1	0
Input B 0	1	1	0
0	1	0	1
1	0	0	1
1	0	0	1
0	1	0	1

All fulfilling table truth table
with OR gate characteristics.

Question 3

~~$Q = (A+B)'$~~
 ~~$Q = \overline{A+B}$~~

~~$Q = A+B$~~

$Q = A'' + B''$
 $= A + B$

A	B	\bar{A}	\bar{B}	\overline{AB}	$\overline{A\bar{B}}$
0	0	1	1	1	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1



OR gate.

1) $A+B = \overline{AB}$

A	B	$A+B$
0	0	0
0	1	1
1	0	1
1	1	1

A	B	\bar{A}	\bar{B}	\overline{AB}	$\overline{A\bar{B}}$
0	0	1	1	1	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1

1) Simplify the following boolean expression

$$\begin{aligned}
 \text{i) } X &= AB + A(B+C) + B(B+C) \\
 &= \underline{AB} + \underline{AB} + \underline{AC} + \underline{BB} + \underline{BC} \\
 &= AB + AC + B + BC \\
 &= AB + AC + B(1+C) \\
 &= \cancel{AB + AC + B} \\
 &= AB + AC + B \\
 &= \cancel{AB} + B + AC \\
 &= \cancel{B(A+1)} + AC \\
 &= B + AC
 \end{aligned}$$

$$\begin{aligned}
 \text{ii) } X &= (A+B)'(C'+D)' \\
 &= (A+B)' + (C'+D)' \\
 &= A'B + CD
 \end{aligned}$$

Question 4
a)

Input			Output
A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$A'BC$

ABC'

ABC

$$X = A'BC + ABC' + ABC$$

b & c)

AB \ C	00	01	11	10
0	0	0	1	0
1	0	1	1	0

$$X = BC + AB$$

(Apply
 $A + A'B = A + B$)

from (a)

$$X = A'BC + ABC' + ABC$$

$$= A'BC + AB(C' + C)$$

$$= A'BC + AB$$

$$= \cancel{A'BC} + B(A + A'C)$$

$$= B(A + C)$$

$$= BC + AB$$

$$X = BC + AB$$